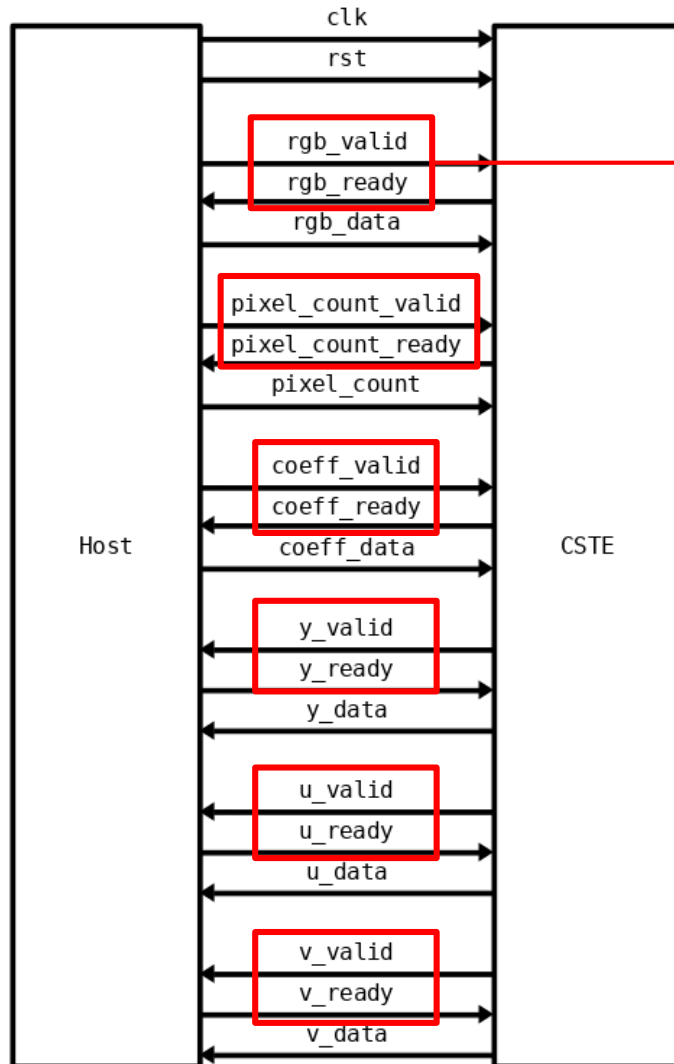


VLSI_Lab

輸入輸出介面


RGB to YUV422



每個資料訊號都有兩個控制訊號 (XX_valid, XX_ready)

輸入輸出介面

 Finish Color Space Transform Engine (CSTE) circuit design



系統描述

YUV Color Space

- Y: 亮度 (Luminance)
- U: 色度 (Chrominance)
- V: 濃度 (Chroma)

$$\begin{aligned}Y &= 0.299 * R + 0.587 * G + 0.114 * B \\U &= -0.169 * R - 0.331 * G + 0.5 * B + 128 \\V &= 0.5 * R - 0.419 * G - 0.081 * B + 128\end{aligned}$$

From Wikipedia

$$\begin{aligned}Y &= (77 * R + 150 * G + 29 * B + 128) \gg 8 \\U &= ((-43 * R - 84 * G + 127 * B + 128) \gg 8) + 128 \\V &= ((127 * R - 106 * G - 21 * B + 128) \gg 8) + 128\end{aligned}$$

From Lab1 Github

定點數(Fix Point)

8 bits for whole number part

8 bits for decimal part

$$0.299 \rightarrow 77$$

$$77_{10} \rightarrow 01001101_2$$

$$0.299 \times 2^8 = 76.544$$

$$2^{-2} + 2^{-5} + 2^{-6} + 2^{-8} = 0.30078125$$

Fix Point 運算

Add / Subtraction

Align the decimal point

Multiplication


Extend bits

Input: 8 bits for whole number part, 8 bits for decimal part


Output: 15 bits for whole number part, 16 bits for decimal part

Keep 16bits


Behavior

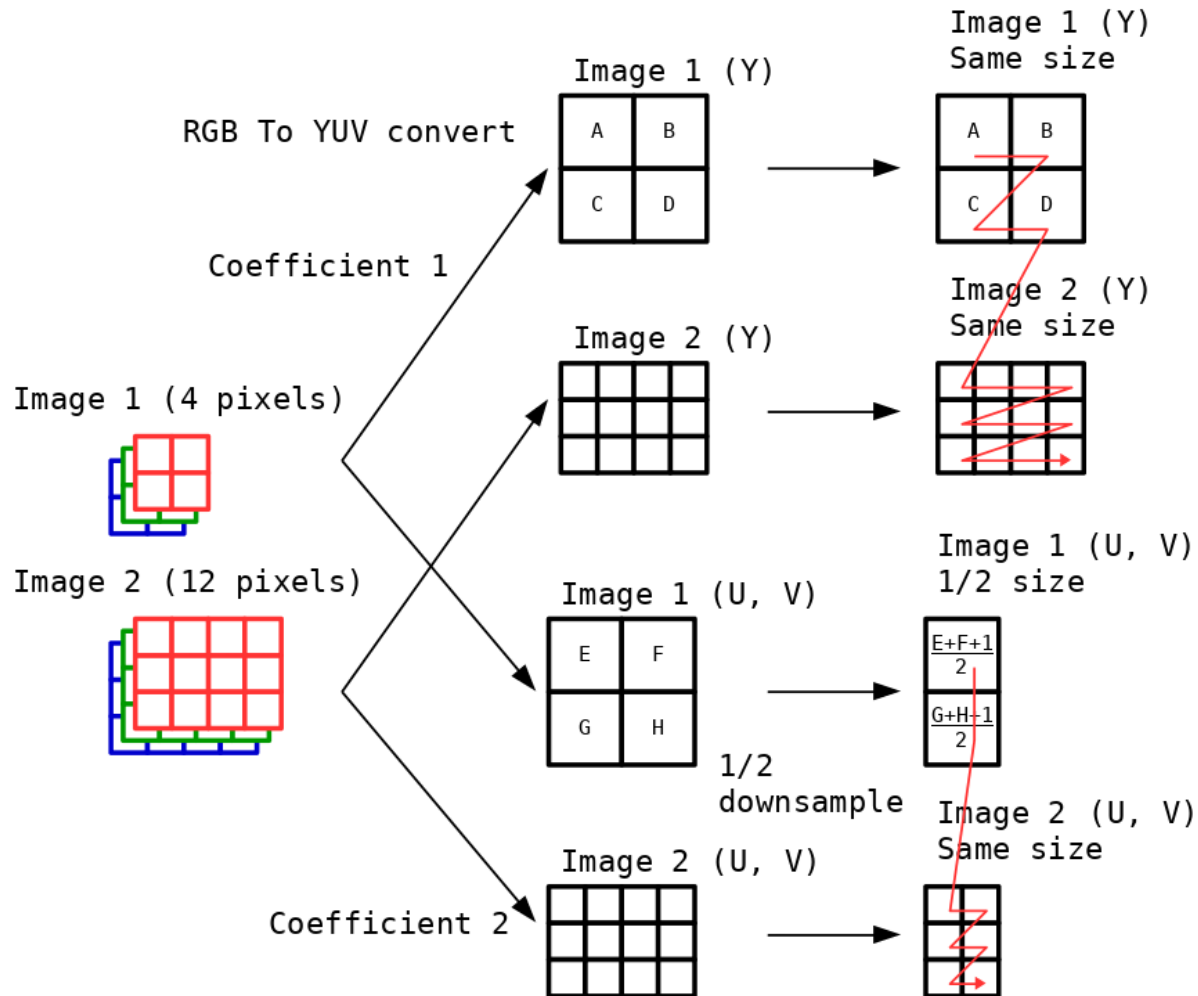

CSTE Over View

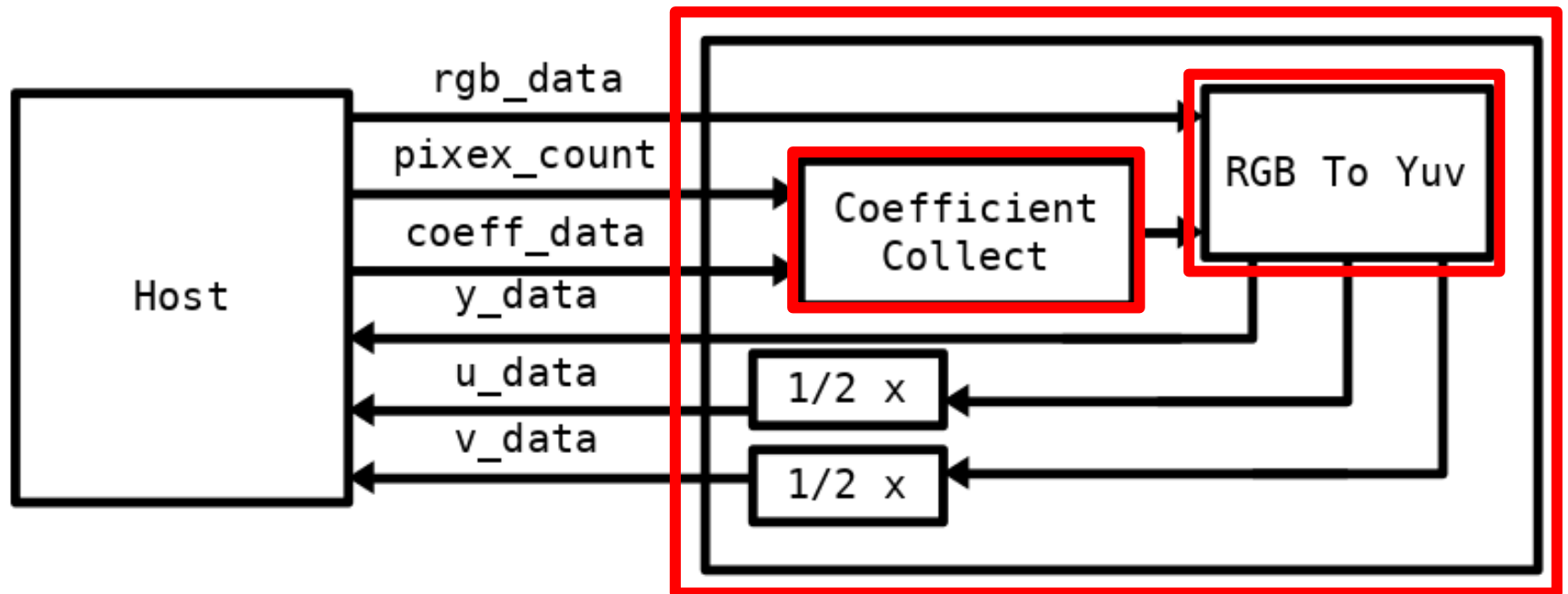

Wave Form

 

Folder

design

- Your design

sim

- Test bench, model

syn

- Gate level synthesis files

Helper.sv

Forward Module

Merge Module



Broadcast Module

AcceptIf Module

IgnoreIf Module

Forward Module

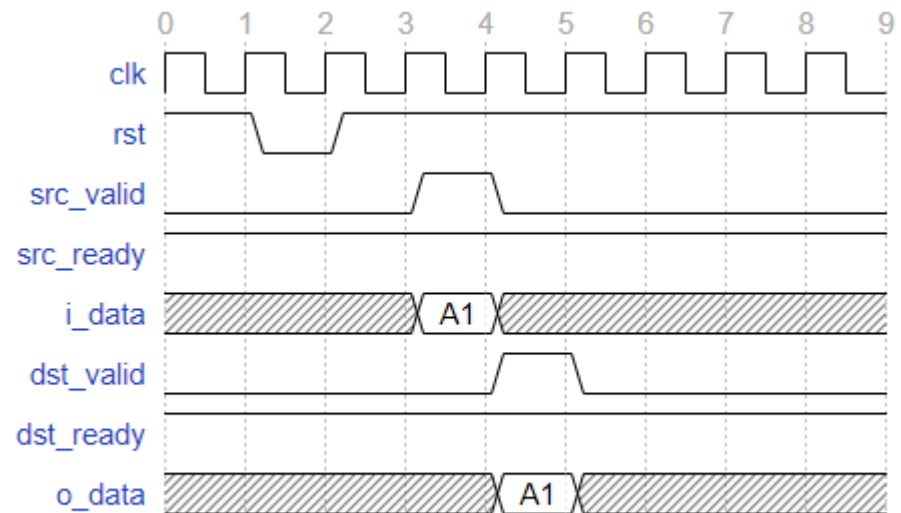 
Forward the handshake protocol signal to the next pipeline stage. This module has to go with **one cycle latency** computation.



Forward-2wire

Forward Module
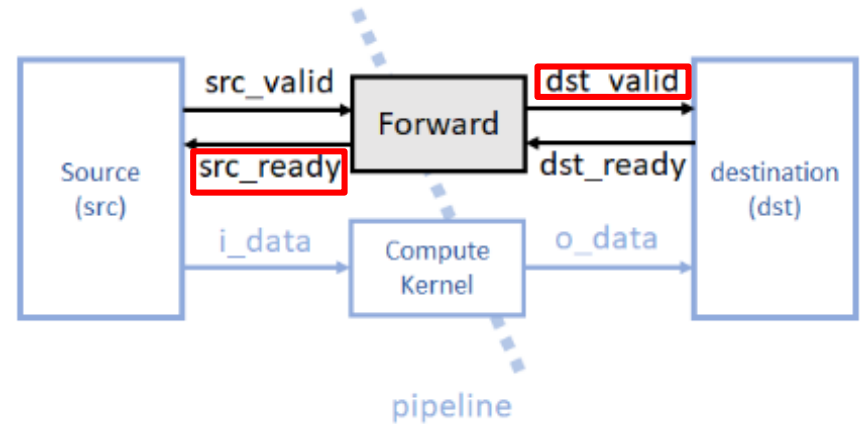
```
module Forward(  
    input logic clk,  
    input logic rst,  
    input logic src_valid,  
    output logic src_ready,  
    output logic dst_valid,  
    input logic dst_ready  
);
```





```
    logic dst_valid_w;    src有data傳過來    data還留在register沒被dst拿走  
    assign dst_valid_w = src_valid || (dst_valid && !dst_ready);  
    assign src_ready = !dst_valid || dst_ready;  
    always_ff @(posedge clk or negedge rst) begin  
        if (!rst) dst_valid <= 1'b0;  
        else dst_valid <= dst_valid_w;  
    end  
endmodule
```

data register是空的

dst 正在拿走 data register 的 data

Merge Module

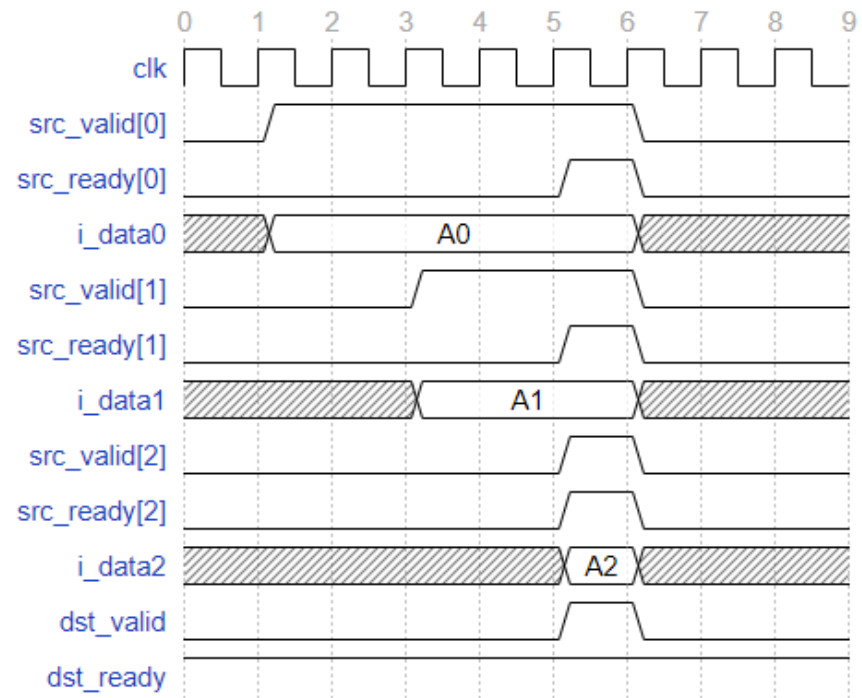 
Handling the control signal between multiple sources and ensuring all the sources sending next input data until all the data from sources are collected.



Merge-2wire, N=3

Merge Module


 
```
module Merge(  
    src_valids,  
    src_readys,  
    dst_valid,  
    dst_ready  
);  
  
    parameter N = 2;  
    input  logic [N-1:0] src_valids;  
    output logic [N-1:0] src_readys;  
    output logic dst_valid;  
    input  logic dst_ready;    所有 src 都準備好  
    assign dst_valid = &src_valids;  
    assign src_readys = {N{dst_valid && dst_ready}};  
endmodule
```



dst 可以拿 data 同時 所有 src 也準備好

Broadcast Module

 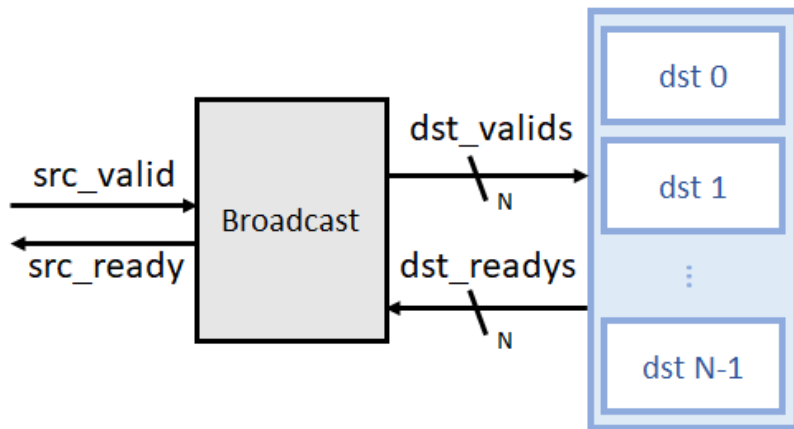Handling the control signal between multiple destinations and ensuring input data remaining the same until all the destinations receiving the valid output data.




拿過 o_data 後, valid 要變成 0

所有 dst 都拿過 o_data 後, 才能拿下一筆 i_data

Broadcast Modul

```
module Broadcast(  
    clk,  
    rst,  
    src_valid,  
    src_ready,  
    dst_valids,  
    dst_readys  
);  
  
    parameter N = 2;  
    input  logic clk;  
    input  logic rst;  
    input  logic src_valid;  
    output logic src_ready;  
    output logic [N-1:0] dst_valids;  
    input  logic [N-1:0] dst_readys;  
    logic [N-1:0] got, got_test, got_w;  
    assign dst_valids = {N{src_valid}} & ~got;  
    assign got_test = got | dst_readys;  
    assign src_ready = &got_test;  
    assign got_w = (src_valid && !src_ready) ? got_test : '0;  
    always_ff @(posedge clk or negedge rst) begin  
        if (!rst) got <= '0;  
        else got <= got_w;  
    end  
endmodule
```

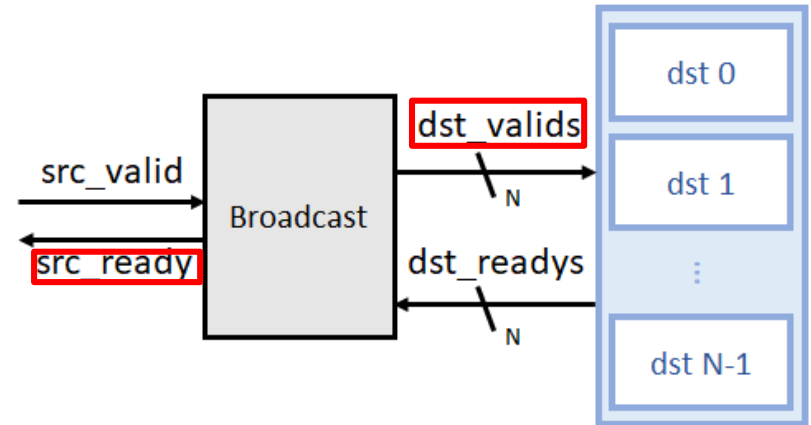

src 準備好，並扣掉拿過的 dst

加上準備要拿 o_data 的 dst

所有 dst 都拿過 o_data 後，才能拿下一筆 i_data

如果還有 dst 還沒拿 o_data → 更新 got


反之 dst 都拿過了或 src 還沒準備好 → got 歸0

記錄哪些 dst 已經拿過 o_data

Ignorelf Module

Skip the src_valid signal to dst_valid when cond is high.

```
module IgnoreIf(  
    input logic cond,  
    input logic src_valid,  
    output logic src_ready,  
    output logic dst_valid,  
    input logic dst_ready,  
    output logic ignore  
);  
  
    parameter bit COND = 1;  
    assign ignore = cond == COND;  
    assign dst_valid = !ignore && src_valid;  
    assign src_ready = ignore || dst_ready;  
endmodule
```

 

ignore=1時，dst_valid必為0

ignore=0時，將src_valid傳給dst_valid

ignore=1時，src_ready必為1，跳過這筆data

ignore=0時，將dst_ready傳給src_ready

AcceptIf Module

Pass the dst_ready to src_ready when condition is high

```
module AcceptIf(  
    input logic cond,  
    input logic src_valid,  
    output logic src_ready,  
    output logic dst_valid,  
    input logic dst_ready,  
    output logic accept  
);  
  
    parameter bit COND = 1;  
    assign accept = cond == COND;  
    assign dst_valid = src_valid;  
    assign src_ready = dst_ready && accept;  
endmodule
```



accept=1時，將dst_ready傳給src_ready
accept=0時，src_ready必為0

TODO

design

1. CoeffCollect

2. RgbToYuv

3. Rgb888ToYuv422

sim

MyModel.py

RgbToYuv_test.py

Rgb888ToYuv422_test.py

CSTE 輸出時序規格

完成電路運算後，欲將資料輸出需將 `y_valid` 設為 `high`，告知 `host` 端有轉換過後的 `pixel` 輸出，本題並未規定需要連續輸出，可自行控制 `y_valid` 控制訊號。(U, V同理)

當所有資料輸出後，系統便會自動結束模擬並檢查。

預設模擬時間約 `2000 cycles`，若屆時未達到足夠筆的資料輸出，系統將輸出 `timeout` 信號。

預設模擬有 `10+18` 個 `pixel`，也就是說必須在 `y_data` 觀察到 `28` 個輸出，`u_data`, `v_data` 看到 `14` 個。

電路測試

本練習電路可以在 `sim/` 資料夾下，輸入以下命令分別測試 `CSTE` 以及 `submodule`。

- `make top`
- `make coeff_col`
- `make rgb2yuv`
- `make downsample`

如果使用 `Verilog` 語法，輸入以下命令

- `make USE_VERILOG=true top`
- `make USE_VERILOG=true coeff_col`
- `make USE_VERILOG=true rgb2yuv`
- `make USE_VERILOG=true downsample`