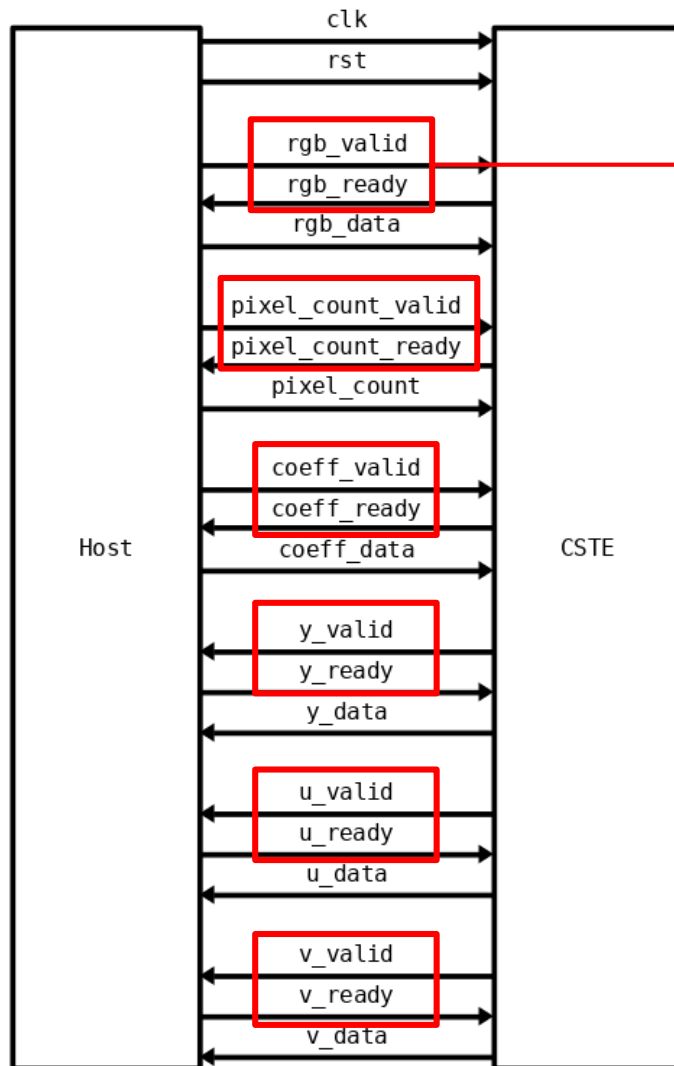


# VLSI\_Lab

---

# 輸入輸出介面

## RGB to YUV422




每個資料訊號都有兩個控制訊號 (XX\_valid, XX\_ready)
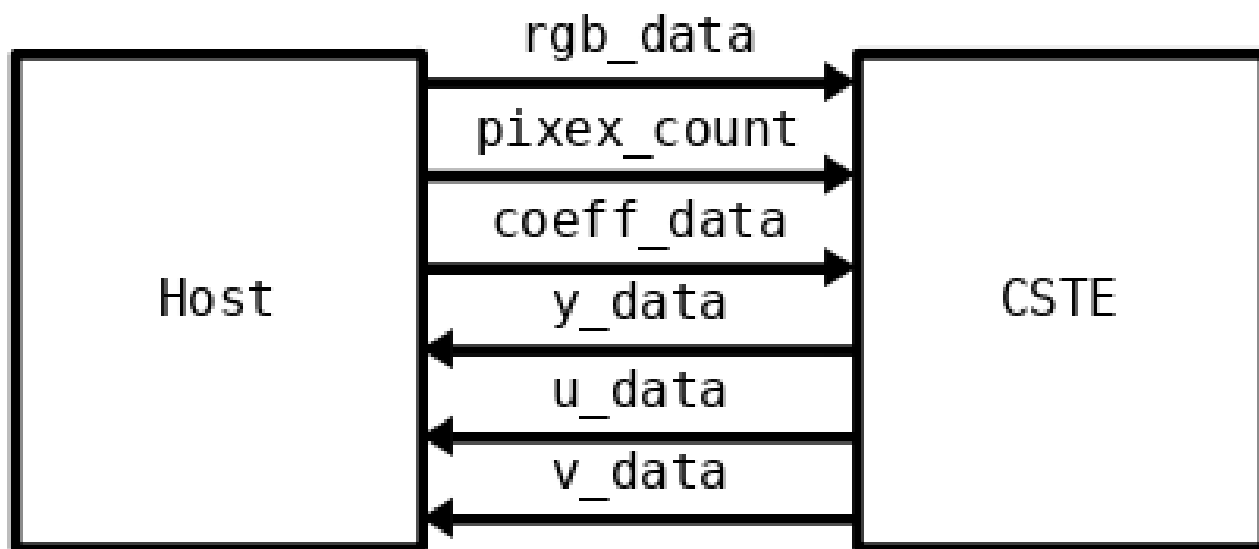
# 輸入輸出介面

---

Finish Color Space Transform Engine (CSTE) circuit design



# 系統描述

---

## YUV Color Space

- Y: 亮度 (Luminance)
- U: 色度 (Chrominance)
- V: 濃度 (Chroma)

$$\begin{aligned}Y &= 0.299 * R + 0.587 * G + 0.114 * B \\U &= -0.169 * R - 0.331 * G + 0.5 * B + 128 \\V &= 0.5 * R - 0.419 * G - 0.081 * B + 128\end{aligned}$$

From Wikipedia

$$\begin{aligned}Y &= (77 * R + 150 * G + 29 * B + 128) \gg 8 \\U &= ((-43 * R - 84 * G + 127 * B + 128) \gg 8) + 128 \\V &= ((127 * R - 106 * G - 21 * B + 128) \gg 8) + 128\end{aligned}$$

From Lab1 Github

# 定點數(Fix Point)

---

8 bits for whole number part

8 bits for decimal part

$$0.299 \rightarrow 77$$

$$77_{10} \rightarrow 01001101_2$$

$$0.299 \times 2^8 = 76.544$$

$$2^{-2} + 2^{-5} + 2^{-6} + 2^{-8} = 0.30078125$$

# Fix Point 運算

---

Add / Subtraction

Align the decimal point

Multiplication


Extend bits

Input: 8 bits for whole number part, 8 bits for decimal part

Output: 15 bits for whole number part, 16 bits for decimal part


Keep 16bits

# Behavior

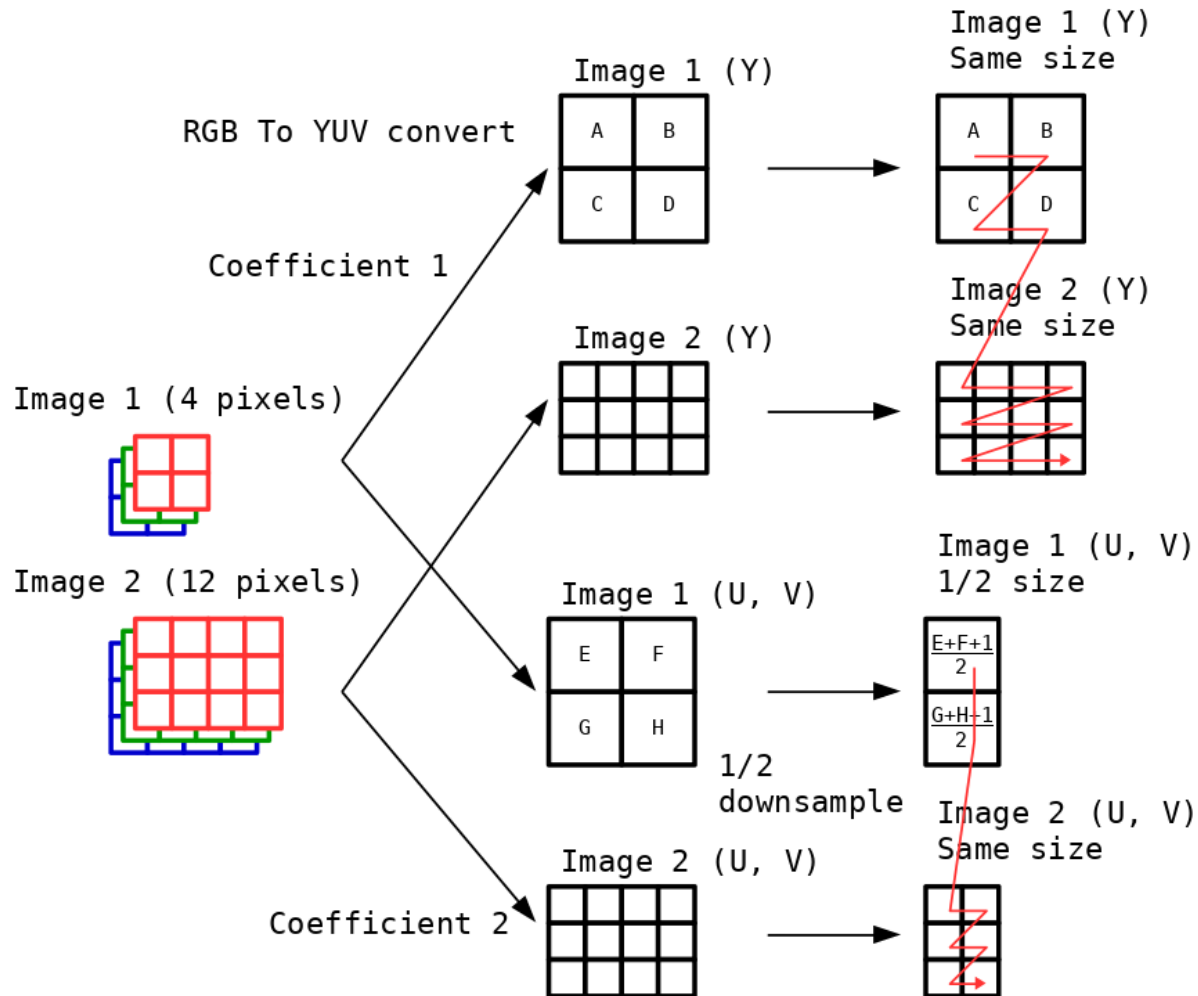


# CSTE Over View

---

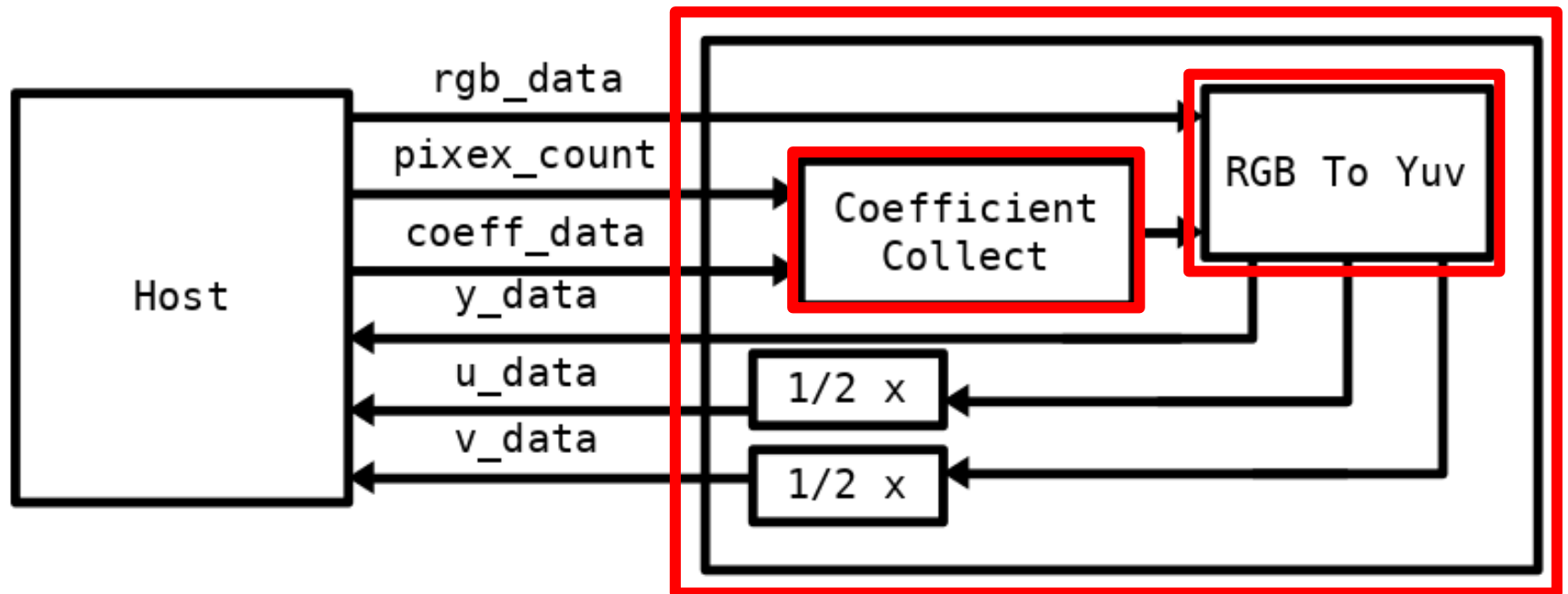



# Wave Form

 

# Folder

---

design

- Your design

sim

- Test bench, model

syn

- Gate level synthesis files

# Helper.sv

---

Forward Module

Merge Module



Broadcast Module

AcceptIf Module

IgnoreIf Module
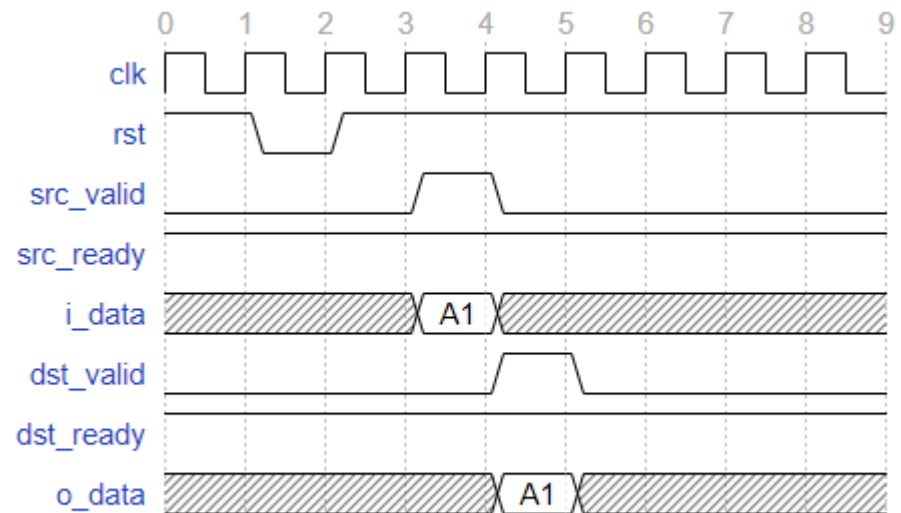 
# Forward Module


Forward the handshake protocol signal to the next pipeline stage. This module has to go with **one cycle latency** computation.



Forward-2wire
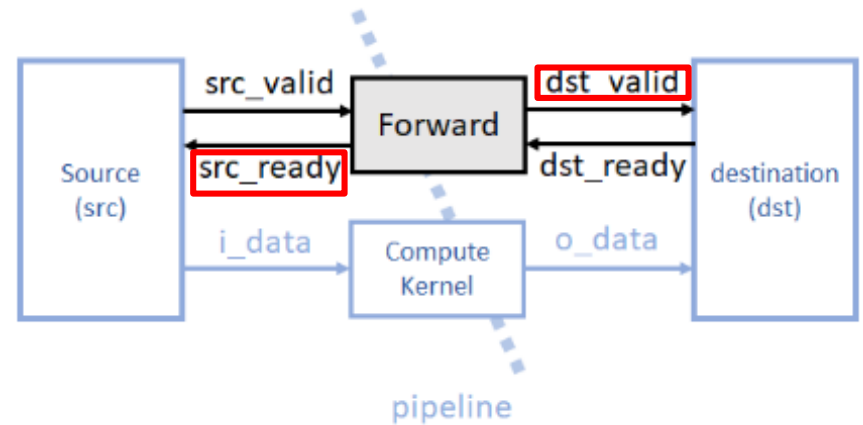
# Forward Module

```
module Forward(  
    input logic clk,  
    input logic rst,  
    input logic src_valid,  
    output logic src_ready,  
    output logic dst_valid,  
    input logic dst_ready  
);
```





```
    logic dst_valid_w;    src有data傳過來    data還留在register沒被dst拿走  
    assign dst_valid_w = src_valid || (dst_valid && !dst_ready);  
    assign src_ready = !dst_valid || dst_ready;  
    always_ff @(posedge clk or negedge rst) begin  
        if (!rst) dst_valid <= 1'b0;  
        else dst_valid <= dst_valid_w;    dst正在拿走 data register 的 data  
    end  
endmodule
```

data register是空的
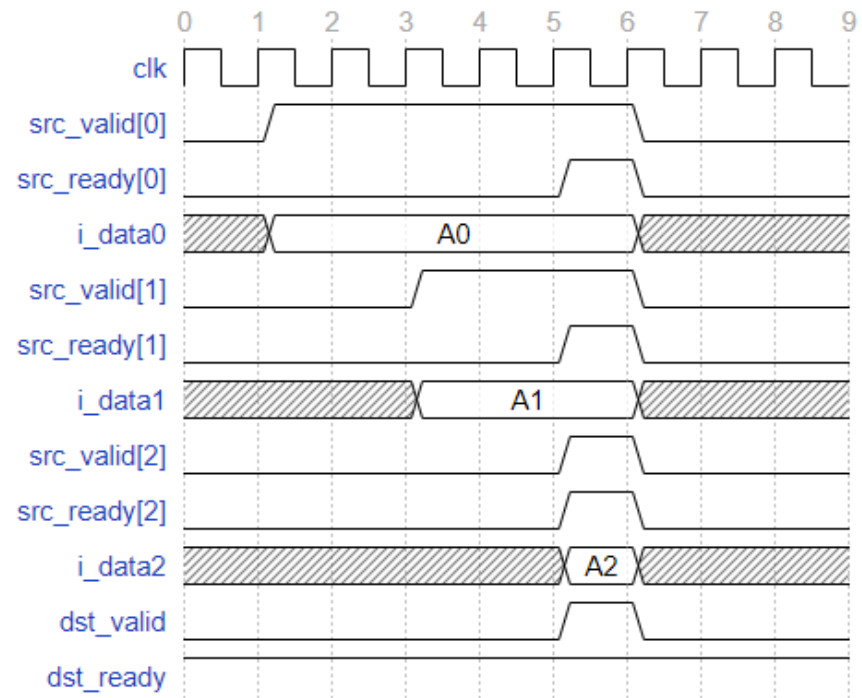 
# Merge Module


Handling the control signal between multiple sources and ensuring all the sources sending next input data until all the data from sources are collected.



Merge-2wire, N=3
 
# Merge Module



```
module Merge(  
    src_valids,  
    src_readys,  
    dst_valid,  
    dst_ready  
);  
  
    parameter N = 2;  
    input  logic [N-1:0] src_valids;  
    output logic [N-1:0] src_readys;  
    output logic dst_valid;  
    input  logic dst_ready;    所有 src 都準備好  
    assign dst_valid = &src_valids;  
    assign src_readys = {N{dst_valid && dst_ready}};  
endmodule
```



dst 可以拿 data 同時 所有 src 也準備好
 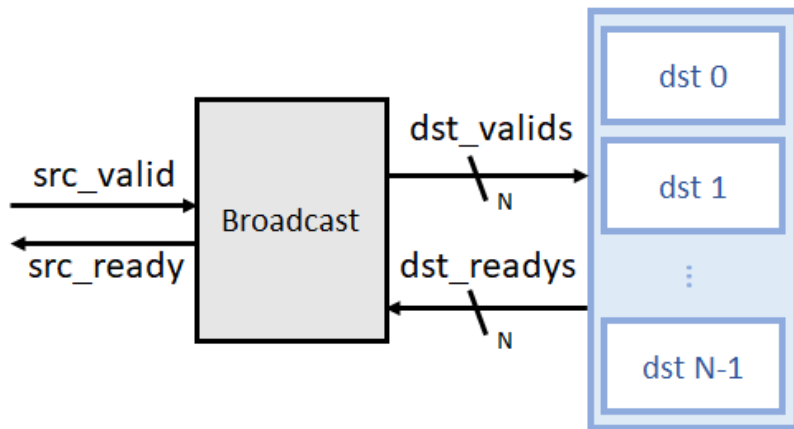
# Broadcast Module

Handling the control signal between multiple destinations and ensuring input data remaining the same until all the destinations receiving the valid output data.




拿過 o\_data 後, valid 要變成 0

所有 dst 都拿過 o\_data 後, 才能拿下一筆 i\_data



# Broadcast Modul

```
module Broadcast(  
    clk,  
    rst,  
    src_valid,  
    src_ready,  
    dst_valids,  
    dst_readys  
);  
  
    parameter N = 2;  
    input  logic clk;  
    input  logic rst;  
    input  logic src_valid;  
    output logic src_ready;  
    output logic [N-1:0] dst_valids;  
    input  logic [N-1:0] dst_readys;  
    logic [N-1:0] got, got_test, got_w;  
    assign dst_valids = {N{src_valid}} & ~got;  
    assign got_test = got | dst_readys;  
    assign src_ready = &got_test;  
    assign got_w = (src_valid && !src_ready) ? got_test : '0;  
    always_ff @(posedge clk or negedge rst) begin  
        if (!rst) got <= '0;  
        else got <= got_w;  
    end  
endmodule
```

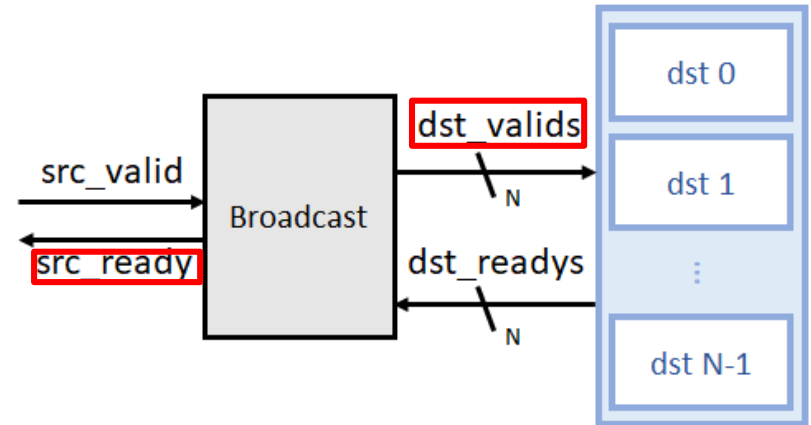

src 準備好，並扣掉拿過的 dst

加上準備要拿 o\_data 的 dst

所有 dst 都拿過 o\_data 後，才能拿下一筆 i\_data

如果還有 dst 還沒拿 o\_data → 更新 got


反之 dst 都拿過了或 src 還沒準備好 → got 歸0

記錄哪些 dst 已經拿過 o\_data

# Ignorelf Module

Skip the src\_valid signal to dst\_valid when cond is high.

```
module IgnoreIf(  
    input  logic cond,  
    input  logic src_valid,  
    output logic src_ready,  
    output logic dst_valid,  
    input  logic dst_ready,  
    output logic ignore  
);  
  
    parameter bit COND = 1;  
    assign ignore = cond == COND;  
    assign dst_valid = !ignore && src_valid;  
    assign src_ready = ignore || dst_ready;  
endmodule
```

 

ignore=1時，dst\_valid必為0

ignore=0時，將src\_valid傳給dst\_valid

ignore=1時，src\_ready必為1，跳過這筆data

ignore=0時，將dst\_ready傳給src\_ready

# AcceptIf Module

Pass the dst\_ready to src\_ready when condition is high

```
module AcceptIf(  
    input logic cond,  
    input logic src_valid,  
    output logic src_ready,  
    output logic dst_valid,  
    input logic dst_ready,  
    output logic accept  
);  
  
    parameter bit COND = 1;  
    assign accept = cond == COND;  
    assign dst_valid = src_valid;  
    assign src_ready = dst_ready && accept;  
endmodule
```



accept=1時，將dst\_ready傳給src\_ready  
accept=0時，src\_ready必為0

# Nicotb

---

- Calculate answer
- Connect to Verilog
- Initialization
- start simulation

# Calculate answer

---

Generate pattern and golden

```
# Calculate answer
coeff_test = M.coeff_test
N_ANS = sum(x[0] for x in coeff_test)
ans = np.vstack(
    np.repeat(np.reshape(c[1], (1,-1)), c[0], axis=0)
    for c in coeff_test
)
```

# Connect to Verilog

---

```
# Connect to Verilog
(
    ivalid, iready,
    ovalid, oready,
    idata, odata,
) = CreateBuses([
    ("dut", "i_valid"),),
    ("dut", "i_ready"),),
    ("dut", "o_valid"),),
    ("dut", "o_ready"),),
    ("dut", "i_data"),),
    ("dut", "o_data"),),
])
```

```
module Downsample(
    input clk,
    input rst,
    // input pixel stream
    input logic      i_valid,
    output logic      i_ready,
    input logic [7:0] i_data,
    // output pixel stream
    output logic      o_valid,
    input logic        o_ready,
    output logic [7:0] o_data
);
```

# Initialization

---

- Define clk and rst even
- Create score board
- Define master and slave
- Extract the data bus of master
- Check the data at slave.

```
rst_out_ev, ck_ev = CreateEvents(["rst_out", "ck_ev"])
```

```
scb = Scoreboard("Counter")  
test = scb.GetTest("Counter")  
st = Stacker(N_ANS, callbacks=[test.Get])  
bg = BusGetter(callbacks=[st.Get])
```

```
master = TwoWire.Master(ivalid, iready, idata, ck_ev, A=1, B=2)  
slave = TwoWire.Slave(ovalid, oready, odata, ck_ev, A=1, B=2, callbacks=[bg.Get])  
mdata = master.values  
test.Expect((gold_out[:, np.newaxis],))
```

# Start simulation

---

```
yield rst_out_ev
yield ck_ev
```

```
def Iter():
    for i in gold_in:
        mdata.i_data[0] = i
        yield mdata
    yield from master.SendIter(Iter())
```

```
for i in range(100):
    yield ck_ev
assert st.is_clean
FinishSim()
```

```
def IterP():
    for i in coeff_test:
        mdatap.pixel_count[0] = i[0]
        yield mdatap

def IterC():
    for i in coeff_test:
        for j in i[1].flat:
            mdatac.coeff_data[0] = j
            yield mdatac

th_1 = JoinableFork(masterp.SendIter(IterP()))
th_2 = JoinableFork(masterc.SendIter(IterC()))
yield from th_1.Join()
yield from th_2.Join()
th_1.Destroy()
th_2.Destroy()
```



# TODO

---

design

1. CoeffCollect

2. RgbToYuv

3. Rgb888ToYuv422

sim

MyModel.py

RgbToYuv\_test.py

Rgb888ToYuv422\_test.py

# CSTE 輸出時序規格

---

完成電路運算後，欲將資料輸出需將 `y_valid` 設為 `high`，告知 `host` 端有轉換過後的 `pixel` 輸出，本題並未規定需要連續輸出，可自行控制 `y_valid` 控制訊號。(U, V同理)

當所有資料輸出後，系統便會自動結束模擬並檢查。

預設模擬時間約 `2000 cycles`，若屆時未達到足夠筆的資料輸出，系統將輸出 `timeout` 信號。

預設模擬有 `10+18` 個 `pixel`，也就是說必須在 `y_data` 觀察到 `28` 個輸出，`u_data`, `v_data` 看到 `14` 個。

# 電路測試

---

本練習電路可以在 `sim/` 資料夾下，輸入以下命令分別測試 `CSTE` 以及 `submodule`。

- `make top`
- `make coeff_col`
- `make rgb2yuv`
- `make downsample`

如果使用 `Verilog` 語法，輸入以下命令

- `make USE_VERILOG=true top`
- `make USE_VERILOG=true coeff_col`
- `make USE_VERILOG=true rgb2yuv`
- `make USE_VERILOG=true downsample`